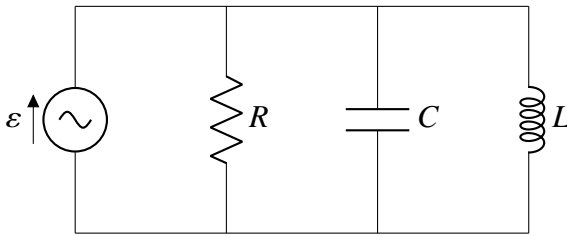


# NCERT ANALOG

## 12.7.17

MANOJ KUMAR (EE23BTECH11211)

**Question 17:** Keeping the source frequency equal to the resonating frequency of the series  $LCR$  circuit, if the three elements,  $L$ ,  $C$ , and  $R$  are arranged in parallel, show that the total current in the parallel  $LCR$  circuit is minimum at this frequency. Obtain the current rms value in each branch of the circuit for the elements and source specified in Exercise 7.11 for this frequency  $\varepsilon = 230V$ ,  $L = 5.0H$ ,  $C = 80\mu F$ ,  $R = 40\Omega$




**Solution:**

Symbol	Value	Description
$L$	$50H$	Inductance
$C$	$80\mu F$	Capacitance
$R$	$40\Omega$	Resistance
$\varepsilon$	$230 V$	Voltage source
$\omega_0$	$\frac{1}{\sqrt{LC}}$	Resonant Angular Frequency
$I_R$	$5.75A$	Rms current value in Resistance
$I_L$	$0.92A$	Rms current value in Inductor
$I_C$	$0.92A$	Rms current value in Capacitor

TABLE 1: Input Parameter

(a)

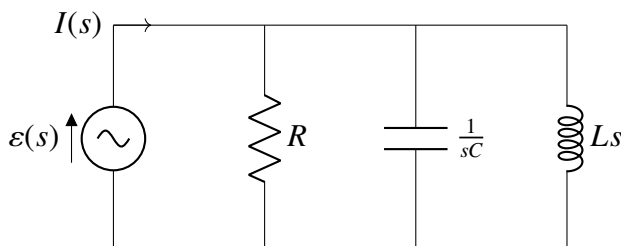

The impedance of the circuit is.

$$\frac{1}{z} = \frac{1}{R} + sC + \frac{1}{Ls} \quad (1)$$

$$I(s) = V(s) \left( \frac{1}{R} + sC + \frac{1}{Ls} \right) \quad (2)$$

At resonance, the circuit becomes purely resistive. The admittance of capacitor and inductor cancel out as follows:

$$sC + \frac{1}{Ls} = 0 \quad (3)$$

$$\Rightarrow s = j \frac{1}{\sqrt{LC}} \quad (4)$$

$s$  can be expressed in terms of angular resonance frequency as

$$s = j\omega_0 \quad (5)$$

Comparing (4) and (5), we get

$$\omega_0 = \frac{1}{\sqrt{LC}} \quad (6)$$

Plot of Impedance vs Angular Frequency  
Impedance is defined as

$$H(s) = \frac{V(s)}{I(s)} \quad (7)$$

Using (5),

$$H(s) = \frac{1}{\frac{1}{R} + sC + \frac{1}{Ls}} \quad (8)$$

$$\Rightarrow H(j\omega) = \frac{1}{\frac{1}{R} + j\omega C + \frac{1}{j\omega L}} \quad (9)$$

$$\Rightarrow |H(j\omega)| = \frac{1}{\sqrt{\frac{1}{R^2} + \left(\omega C - \frac{1}{\omega L}\right)^2}} \quad (10)$$

Hence it is proved that in parallel RLC circuit the total current is minimum at resonance frequency

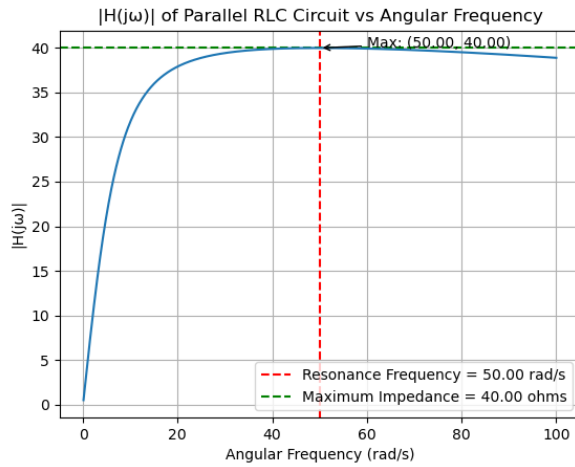


Fig. 0: Maximum impedance at resonating frequency in parallel RLC circuit

(b)

At resonance frequency, Rms currents are

$$\omega_0 = \frac{1}{\sqrt{LC}} = 50 \text{ rad/s} \quad (11)$$

$$I_L = \frac{V}{\omega_0 L} = \frac{230}{250} = 0.92 \text{ A} \quad (12)$$

$$I_C = \omega_0 C V = 0.92 \text{ A} \quad (13)$$

$$I_R = \frac{V}{R} = \frac{230}{40} = 5.75 \text{ A} \quad (14)$$